
Birthday Countdown Timer

By Joseph Cabrera

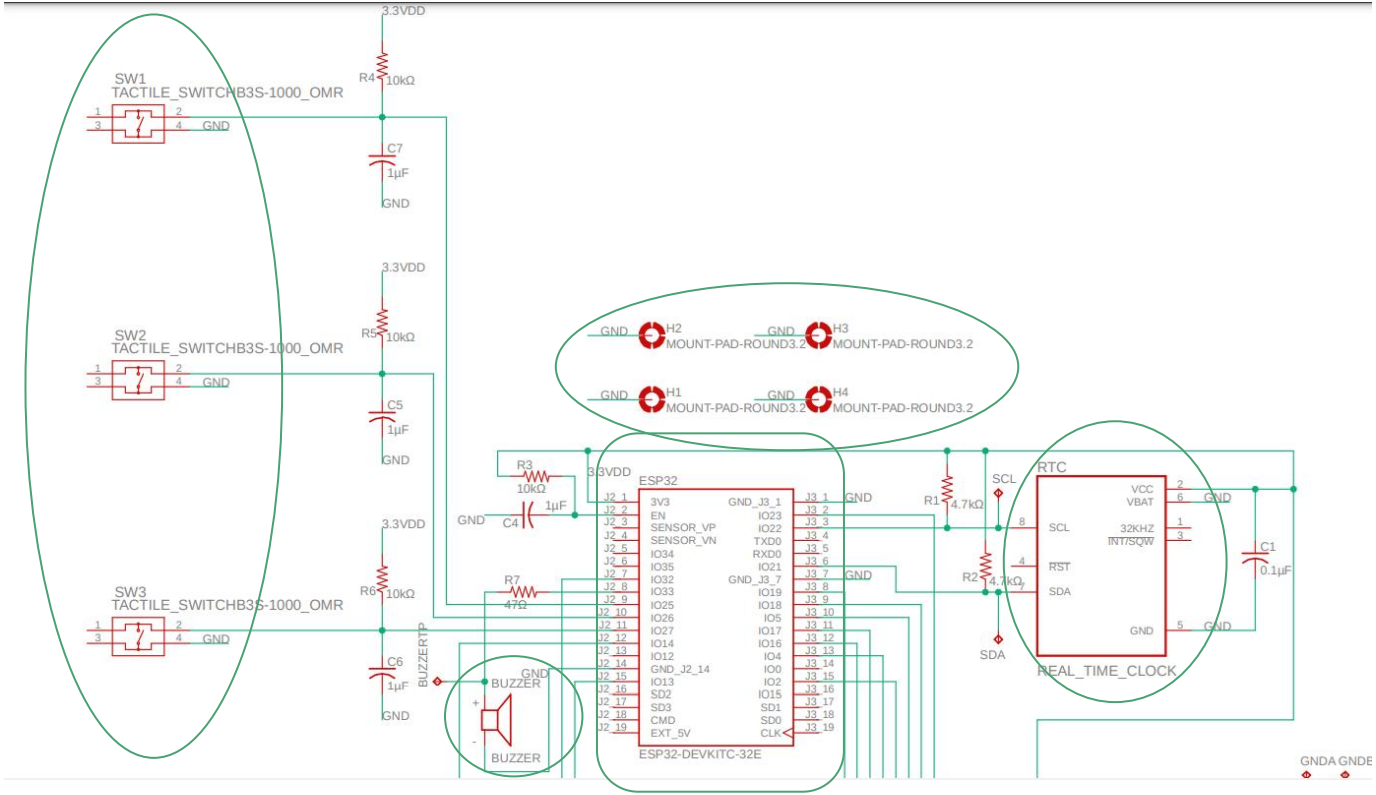


Schematic Diagram Pt. 1

- ESP32-Devkit
- 3 Pushbuttons
- Buzzer
- Real-Time Clock
- Grounded Mounting Holes




Schematic Diagram Pt.2

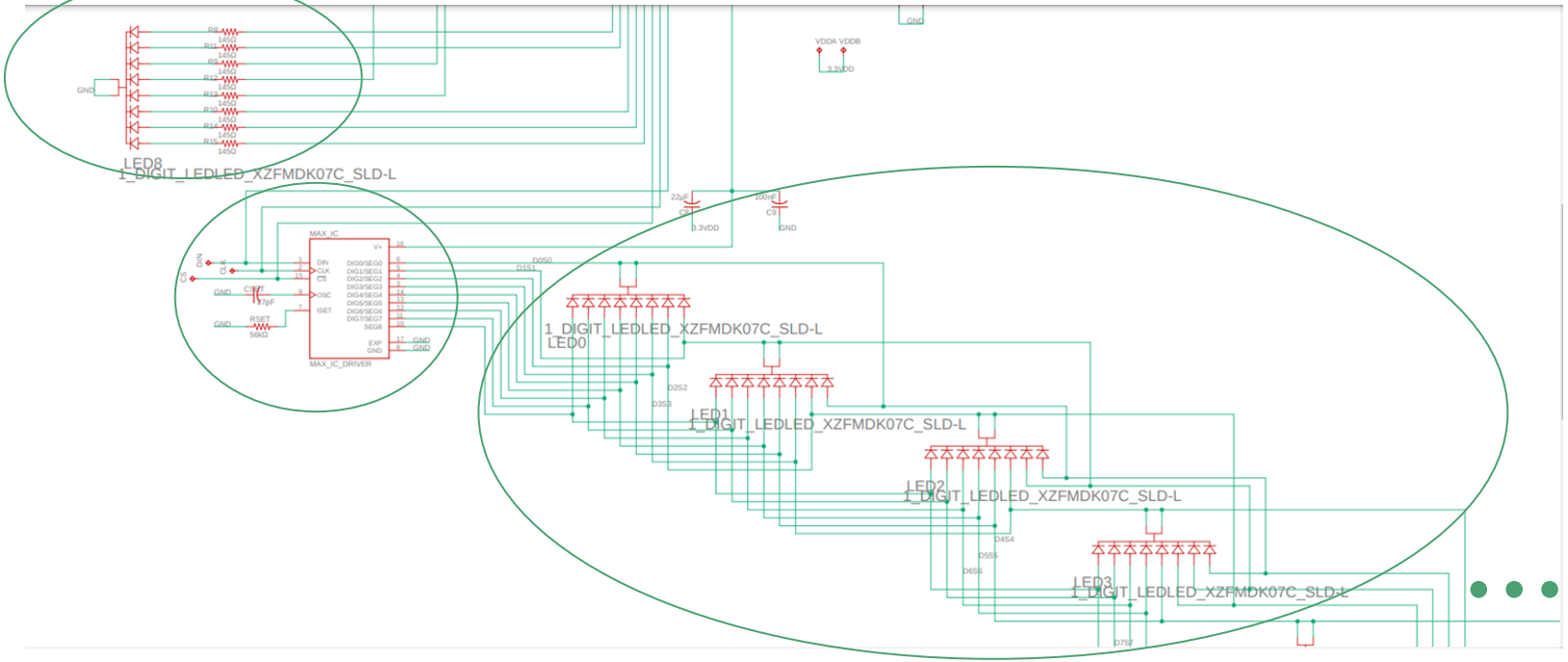


- 7-segment LED connected directly to ESP32-Devkit
- Eight 7-segment LEDs driven by display driver
- Display Driver

Board Layout

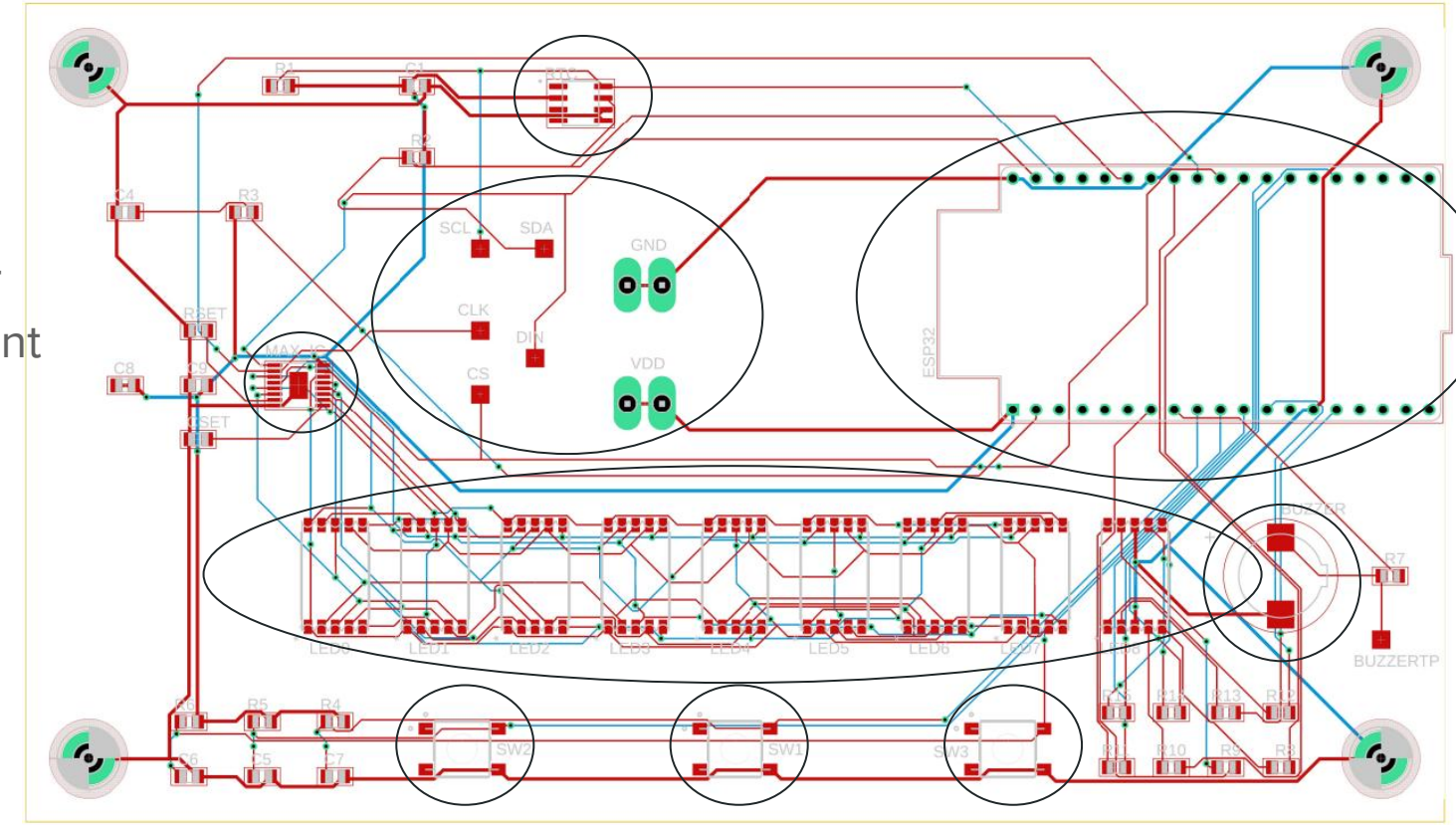- ESP32-Devkit
- Real-Time Clock
- Display Driver
- Nine 7-segment LEDs
- Three Pushbuttons
- Buzzer
- Test Points



Board Photos

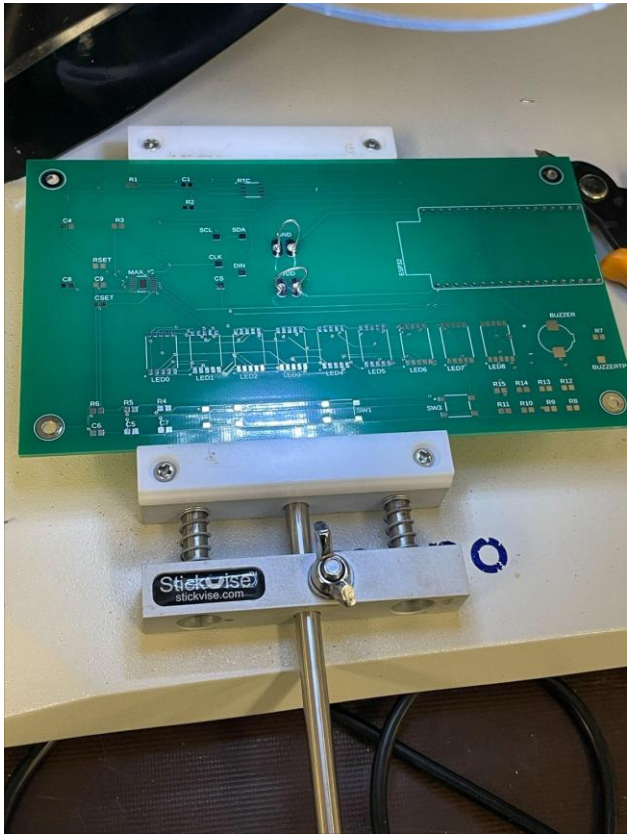




Case Design (Bottom)


- Four screw holes diameter of 2.6mm


- Micro USB insert hole

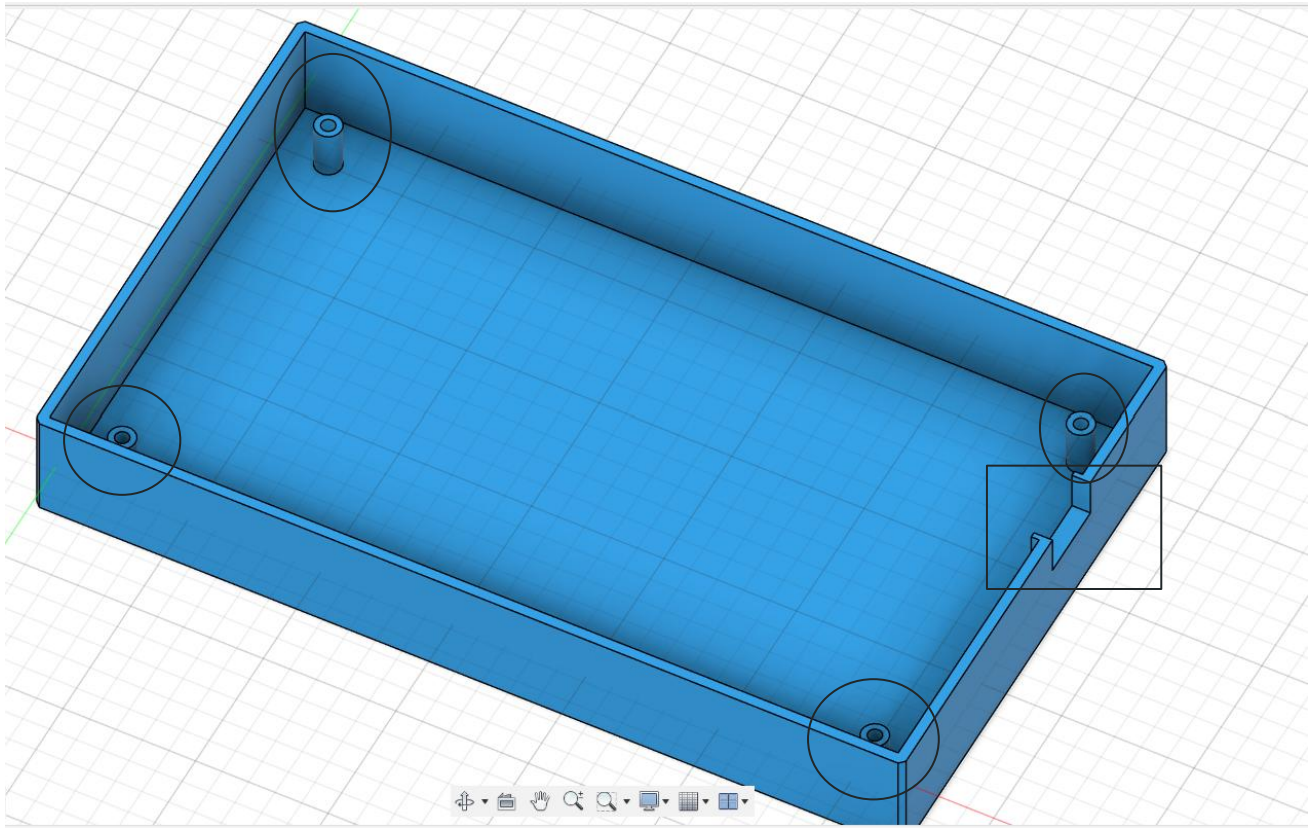

Case Design (Top)

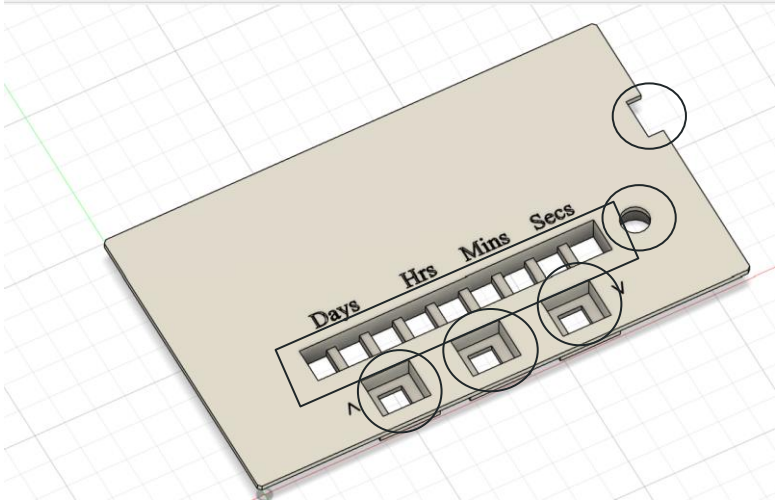- Four tangential pins for connecting to the bottom



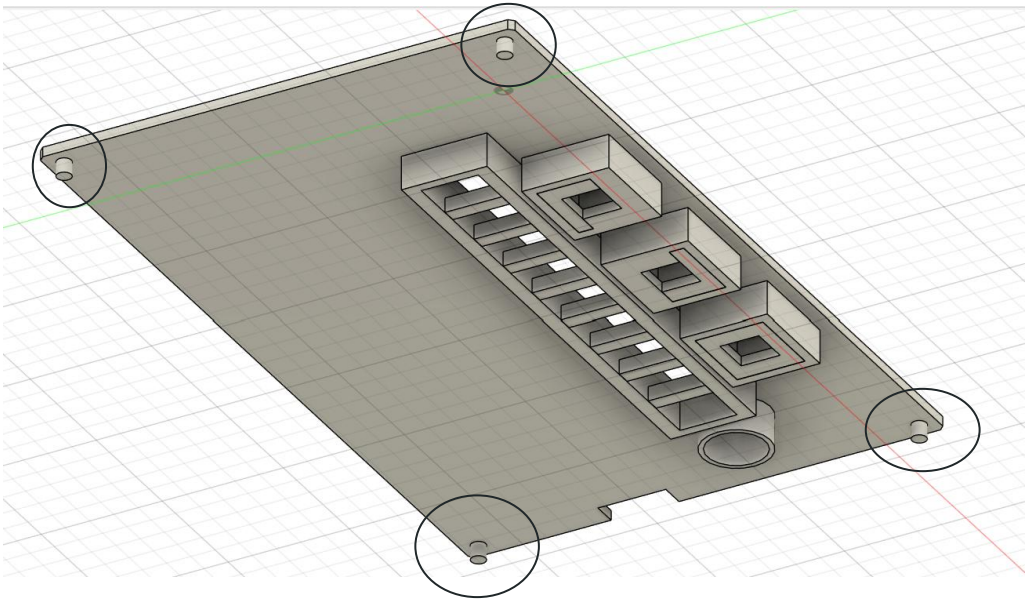

- Holes for 7-segment LEDs
- Holes for pushbuttons
- Hole for the buzzer
- Indent for micro USB
- Some text

Results

